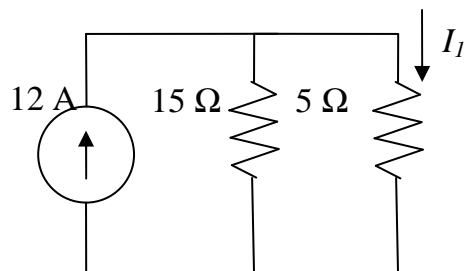


Problem 1 [15 points]: Circuit Basics

a) Multiple Choice Questions. Select only ONE choice. No credit will be given to multiple answers. [5 pts each]


1) What is the current in I_I ?

- a) 3 A
- b) 6 A
- c) 9 A
- d) 12 A




2) Which element is absorbing power?

- a) #1
- b) #2

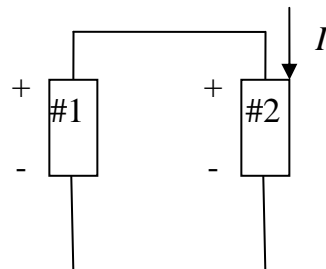


3) If $V_1 = 2$ V, $V_2 = -3$ V, $V_3 = 5$ V, $V_4 = 5$ V, what is V_5 ?

- a) 8 V
- b) 2 V
- c) -8 V
- d) -2 V

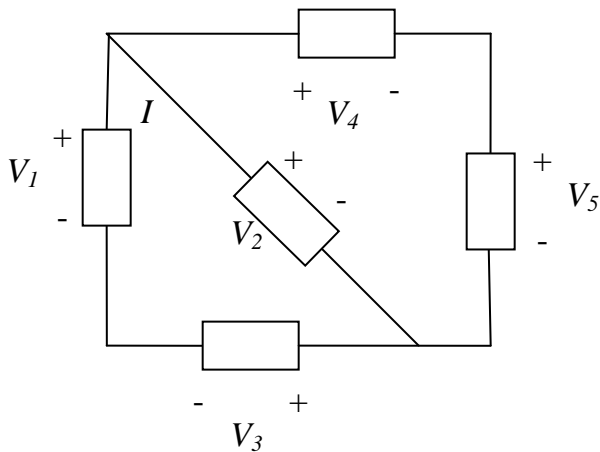

Problem 2 [20 points]: Circuit Basics

1) Consider the circuit below:

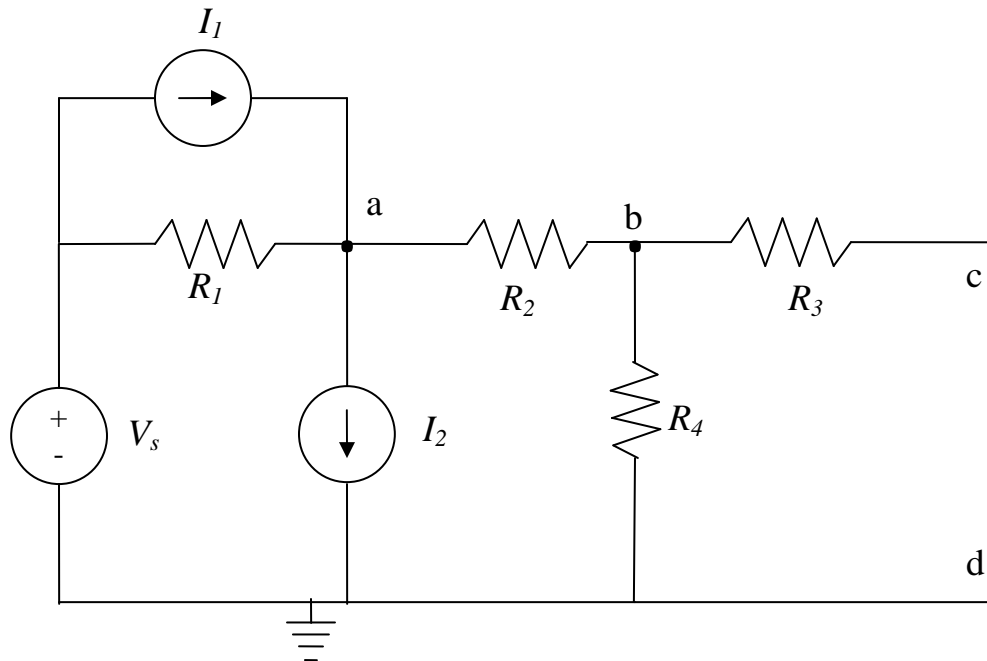


a) Write a KCL expression for node a . Be sure to label any new variables you create on the circuit diagram above. [5 pts]

b) Write a KCL expression for node b . Be sure to label any new variables you create on the circuit diagram above. [5 pts]


c) What is R_{TH} between nodes c and d ? [5 pts]

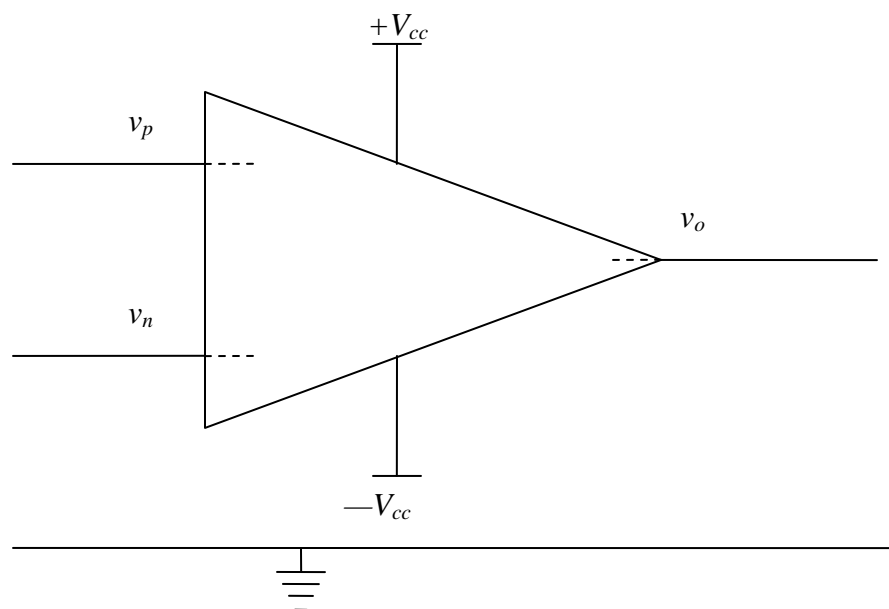2.) Draw the equivalent circuit model of an op amp in the linear range: **[5 pts]**
Be sure to label all the elements.



Problem 3 [24 points]: Maximum Power Transfer

Consider the circuit below:

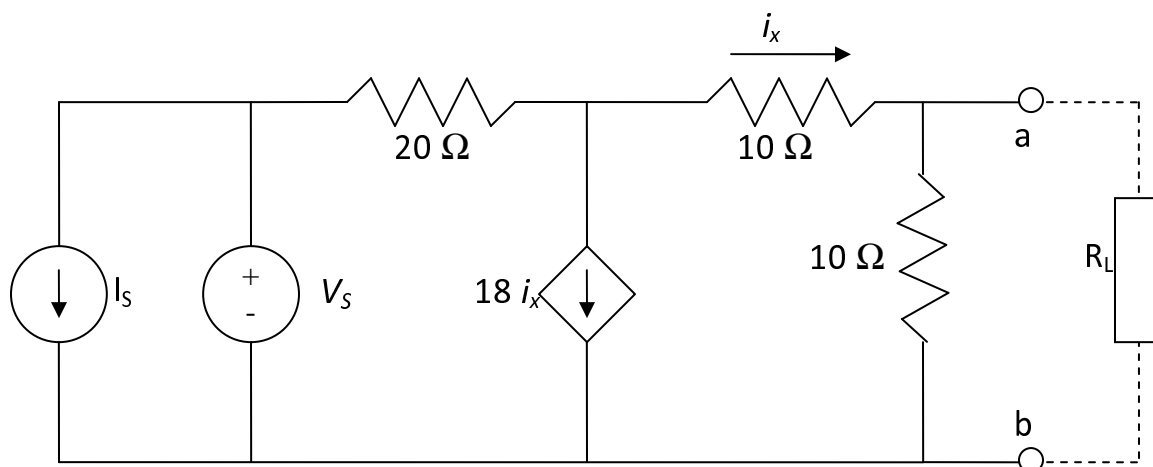

a.) Find the Thévenin equivalent between a and b [12 pts]

For parts (b) to (d), please use the values $V_{TH} = 5 \text{ V}$ and $R_{TH} = 1\text{k}\Omega$ INSTEAD of the values you found in part (a).


b.) Find the Norton equivalent between a and b **[6 pts]**

c.) Based on your answer in part (b), find the optimal R_L such that the power delivered to R_L is maximized. **[3 pts]**

d.) Based on your answer to part (c), what power is dissipated by R_L ? **[3 pts]**

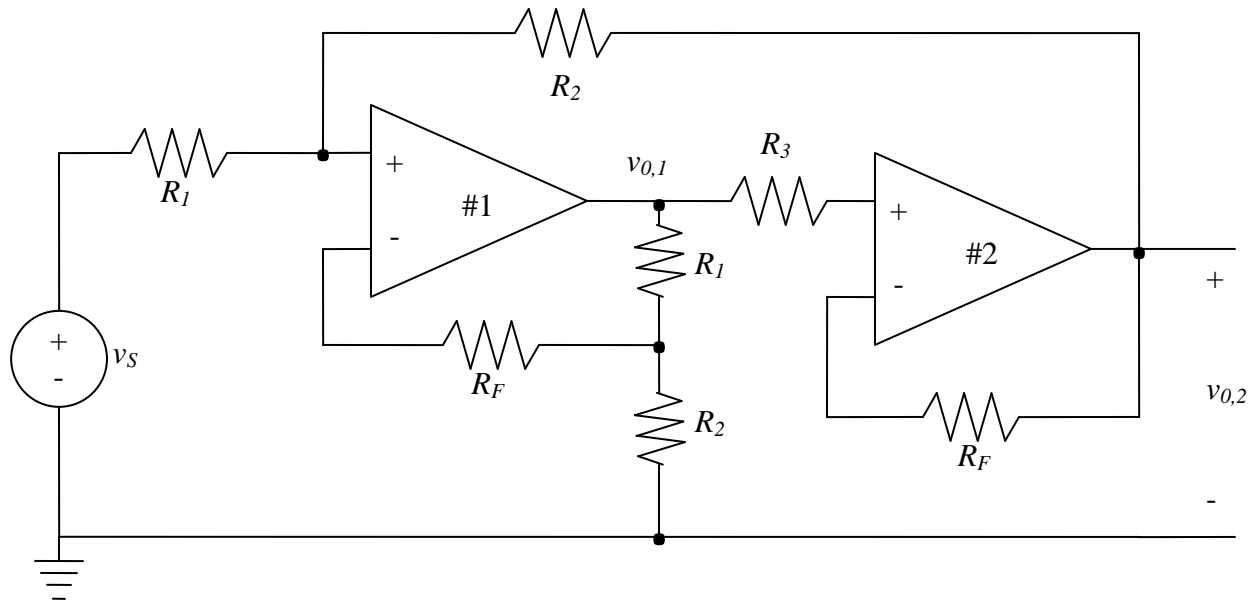Problem 4 [20 points]: Op Amp Circuit

Consider the circuit below. Assume that both op-amps are ideal.



a) Write the KCL expression at the non-inverting input of op-amp #1. Be sure to label any new variables you create on the circuit diagram above. [8 pts]

b) Find the expression for the overall gain, $G = v_{0,2}/v_s$ in terms of the listed parameters. [12 pts]

Problem 5 [16 points]: EE Technology and Circuit Basics

True or False Questions. Select only ONE answer. [2 pts each]

- | | | |
|---|---|---|
| T | F | Moore's Law describes the phenomenon where the number of transistors on a computer chip doubles every 1.5 to 2 years. |
| T | F | The state-of-the-art solid-state transistor has dimensions on the order of $450\text{ }\mu\text{m}$. |
| T | F | The maximum power that a solar cell can deliver in practice can be determined by $i_{sc} \times v_{oc}$. |
| T | F | A good voltage source should have a small series resistance. |
| T | F | Any linear circuit can be reduced to an equivalent circuit comprising a voltage source with a series resistance. |
| T | F | The equivalent circuit from the previous question is called a Norton equivalent |
| T | F | A Wheatstone bridge is a circuit that can be used to measure change in resistance of a resistive sensor. |
| T | F | Multisim is a circuit simulator based on SPICE: Simulation Program with Integrated Circuit Emphasis. |