

Problem 1: Design an RC low-pass filter with a pole at 10^6 radians/sec.

a) Draw the filter, and label input and the output, and the capacitor and resistor values.


P1	/20
P2	/20
P3	/20
P4	/20
P5	/20
Total	/100

b) if you drive the input to your filter with $V_{in}(t) = \sin(10^6 t) + 5 \sin(100t) + 10 \sin(10^7 t)$, what will the output waveform be?

$V_{out} =$

c) **Carefully** sketch a single cycle of the input and output sine waves for $V_{in} = \sin(10^6 t)$. I want it to be very clear what the magnitude and phase of the output is relative to the input. **Label the axes clearly.**

$V_{in} = \sin(10^6 t)$

 

Problem 2: Assume room temperature for this problem.

A pn junction has $N_D=10^{20} \text{ cm}^{-3}$ and $N_A=10^{15} \text{ cm}^{-3}$

a) What is the built-in potential V_0 ?

$V_0 =$

b) What is the approximate concentration of n and p carriers on each side of the junction?

$n_n =$

$p_n =$

$n_p =$

$p_p =$

c) For a particular junction area, the total zero-bias capacitance is measured to be $C(0V) = 10\text{pF}$. With a reverse bias of 10V, what is the approximate capacitance of this particular junction?

$C(-10V) =$

d) In a different junction with the same area, the donor concentration is decreased 10x to $N_D=10^{19} \text{ cm}^{-3}$, and the acceptor concentration is increased 10x to $N_A=10^{16} \text{ cm}^{-3}$. What is the change in the built-in potential?

What is the approximate change in the zero-bias capacitance?

$V_0 =$

$C(0V) =$

e) When you forward bias a particular diode at 700mV you measure a current of 0.5mA. What bias voltage is needed to achieve a current of 5mA? What bias voltage is needed to achieve a current of 10mA? Your answers should be accurate to within 5mV.

$V_{BE}(5\text{mA}) =$

$V_{BE}(10\text{mA}) =$

Problem 3:

a) Assuming that $T=300\text{K}$, what is V_{TH} ? (to within 1mV)

$V_{\text{TH}}=$

Approximately what is $V_{\text{TH}} \ln(10)$? (to within 1mV)

$V_{\text{TH}} \ln(10)=$

Approximately what is $\exp(60\text{mV}/V_{\text{TH}})$? (to within 5%)

$\exp(60\text{mV}/V_{\text{TH}})=$

b) In a bipolar junction transistor, most of the current flow through the base region is due to (circle one) **majority** or **minority** carriers?

These carriers move mostly due to (circle one) **drift** or **diffusion**?



c) In a MOSFET, most of the current flowing in the channel region is due to (circle one) **majority** or **minority** carriers?

These carriers move mostly due to (circle one) **drift** or **diffusion**?

Problem 4: Carefully draw the normal IV curves for an NPN BJT and an NMOS FET with the following assumptions:

- a) For the BJT, $I_S=10^{-18}$ A, $V_A=50$ V. Draw the curves for $V_{BE} = 600$ mV, 620 mV, 640 mV, 660 mV with V_{CE} running from 0 to 5 V.
- b) For the FET, $\mu_n C_{ox}=200$ μ A/V², $V_t = 0.5$ V, $\lambda=0.05$ V⁻¹, $W/L=5\mu/0.5\mu$. Draw the curves for $V_{GS} = 0.5$, 1.5, 2.5, 3.5 V, with V_{DS} running from 0 to 5 V.

Clearly label all curves and axes.

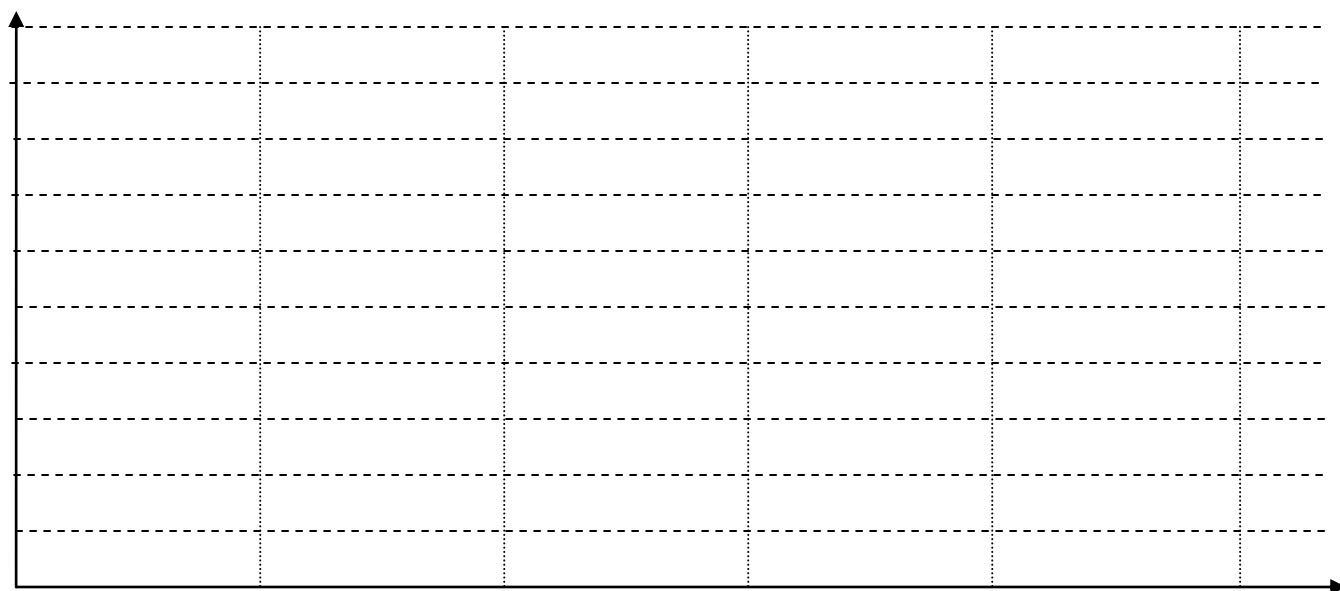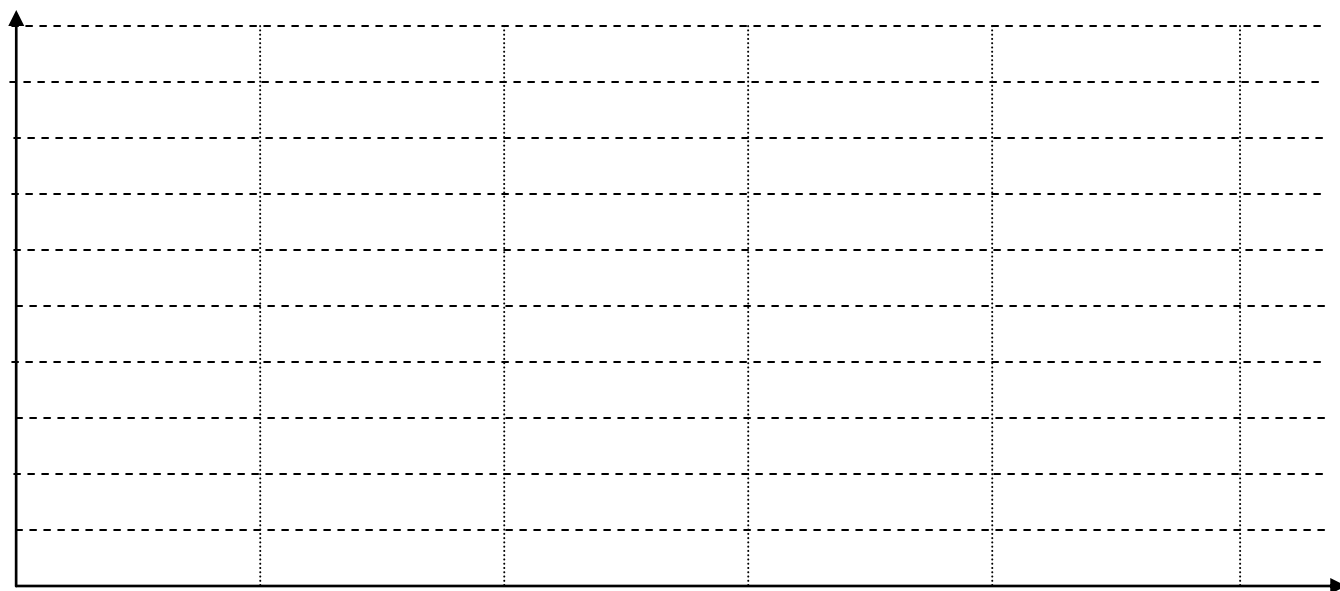

Problem 5:

a) For a BJT with the same specs as in the previous problem, when $I_C = 1\mu\text{A}$, calculate the small-signal parameters and draw the small-signal model. Assume $\beta=100$.

parameters	model

b) For a MOSFET with the same specs as in the previous problem, when $I_D = 12.5\mu\text{A}$ and $V_{DS}=5\text{V}$, calculate the small-signal parameters and draw the small-signal model.

Clearly label all circuit elements and terminals.

parameters	model