

UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering and Computer Sciences

EE40
Summer 09

Frank Liao

MIDTERM EXAMINATION #1

Time allotted: 90 minutes

NAME: SOLUTIONS
(print) Last First

STUDENT ID#: _____

DISCUSSION SECTION: _____ / _____
Day / Time

LAB SECTION: _____ / _____
Days / Time

INSTRUCTIONS:

1. **SHOW YOUR WORK.** Partial credit will be given only if your methods are clear to the grader.
2. Clearly mark (BOX or UNDERLINE) your answers.
3. Specify the units on answers whenever appropriate. Points will be deducted for missing units.
4. Closed book, closed notes. You are allowed ONE 8.5" x 11" sheet of notes.
5. Calculators are allowed.

I acknowledge that the UC rules on academic honesty apply. _____
Signature

SCORE: 1 _____ / 15
2 _____ / 20
3 _____ / 24
4 _____ / 20
5 _____ / 16 TOTAL: _____ / 95


SOLUTIONS

Problem 1 [15 points]: Circuit Basics

a) Multiple Choice Questions. Select only ONE choice. No credit will be given to multiple answers. [5 pts each]


1) What is the current in I_I ?

- a) 3 A
- b) 6 A
- c) 9 A
- d) 12 A

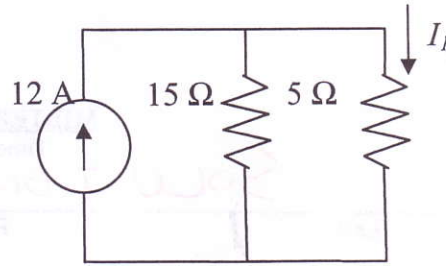


2) Which element is absorbing power?

- a) #1
- b) #2

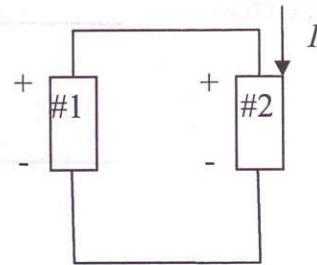

3) If $V_1 = 2$ V, $V_2 = -3$ V, $V_3 = 5$ V, $V_4 = 5$ V, what is V_5 ?


- a) 8 V
- b) 2 V
- c) -8 V
- d) -2 V

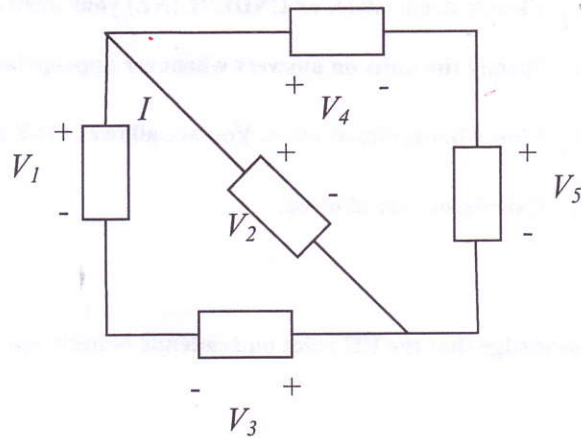

SOLUTIONS

Problem 2 [20 points]: Circuit Basics

1) Consider the circuit below:

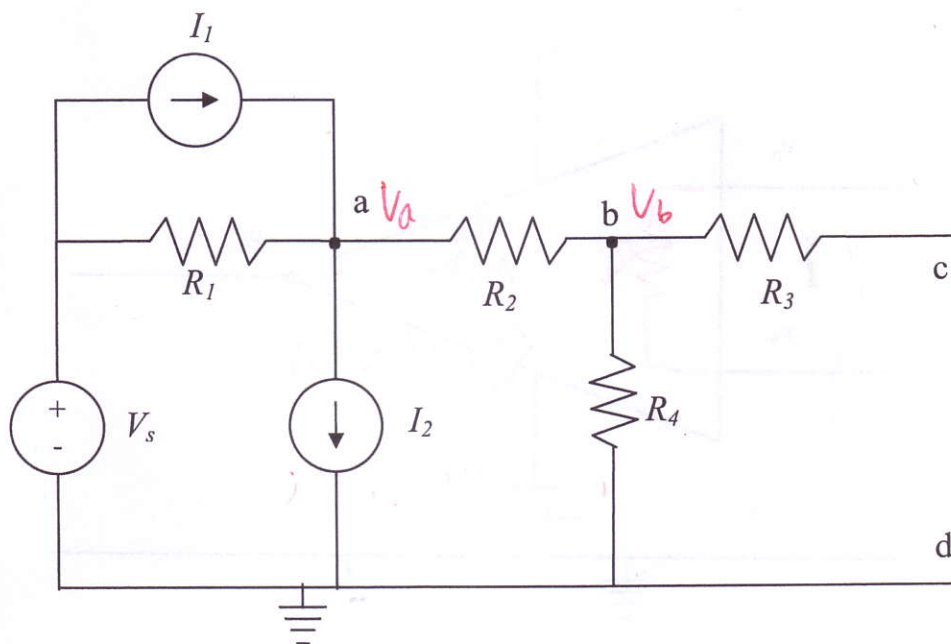

a) Write a KCL expression for node a . Be sure to label any new variables you create on the circuit diagram above. [5 pts]

$$\frac{V_a - V_s}{R_1} + \frac{V_a - V_b}{R_2} + I_2 - I_1 = 0$$

flipped signs = -1 each (max 2)

omit a voltage in a term = -1 each



b) Write a KCL expression for node b . Be sure to label any new variables you create on the circuit diagram above. [5 pts]

$$0 = \frac{V_b - V_a}{R_2} + \frac{V_b}{R_4}$$

include R_3 term = -1

Flip sign = -1

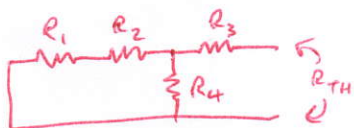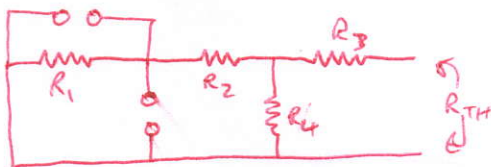c) What is R_{TH} between nodes c and d ? [5 pts]



$$R_{TH} = (R_1 + R_2) \parallel R_4 + R_3$$

$$= \frac{1}{\frac{1}{R_1 + R_2} + \frac{1}{R_4}} + R_3$$

$$= \frac{(R_1 + R_2) R_4}{R_1 + R_2 + R_4} + R_3$$


miss reciprocal = -1 each

open all supplies = 0

miss R_3 = -1

SOLUTIONS

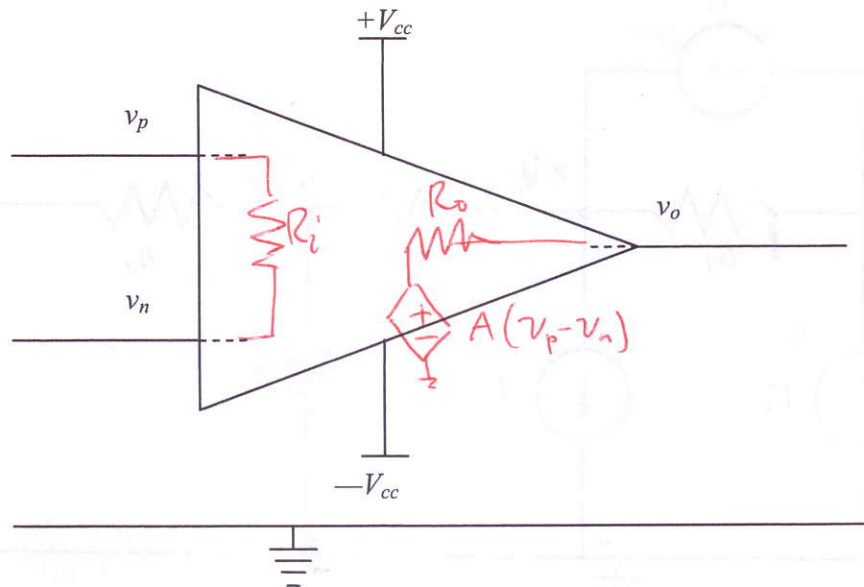
2.) Draw the equivalent circuit model of an op amp in the linear range: [5 pts]
Be sure to label all the elements.



SOLUTIONS

Problem 3 [24 points]: Maximum Power Transfer

Consider the circuit below:

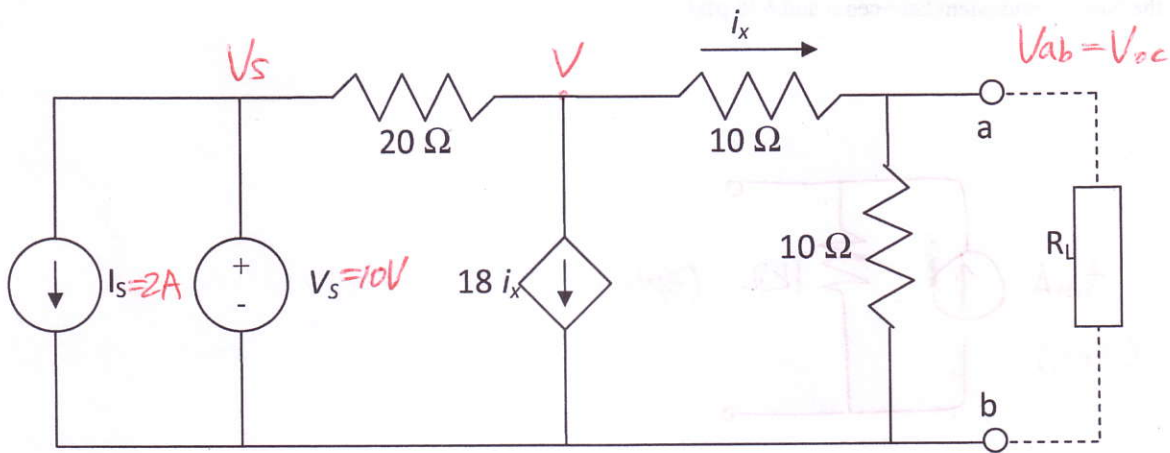

a.) Find the Thévenin equivalent between \$a\$ and \$b\$ [12 pts]

For \$V_{Th}\$

KCL


$$\frac{V - V_s}{20} + 18i_x + \frac{V}{10 + 10} = 0 \quad (2pts)$$

$$i_x = \frac{V}{10 + 10} = \frac{V}{20} \quad (1.5pts)$$

$$\therefore V = \frac{V_s}{20}, \quad V_{Th} = V_{oc} = \frac{10}{10 + 10} V = \frac{1}{2} \frac{V_s}{20} = \frac{1}{40} V_s \quad (2pts)$$

$$= 0.25 V$$

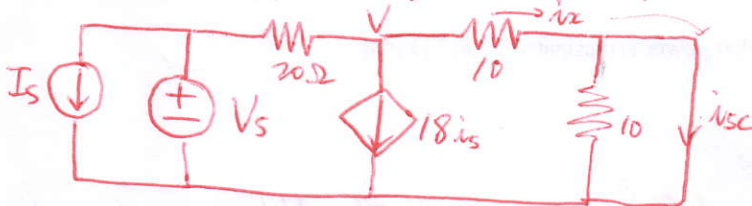For \$R_{Th}\$, we can use short-circuit method.




$$\text{KCL} \quad \frac{V - V_s}{20} + \frac{V}{10} + 18 \frac{V}{10} = 0 \quad (2pts)$$

$$i_x = \frac{V}{10} = i_{sc} \quad (1.5pts)$$

$$\therefore V = \frac{V_s}{39}, \quad i_{sc} = \frac{V_s}{390} = \frac{1}{39} \quad R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{\frac{1}{40} V_s}{\frac{1}{390} V_s} = \frac{39}{4} \Omega \quad (2pts)$$


$$= 9.75 \Omega$$

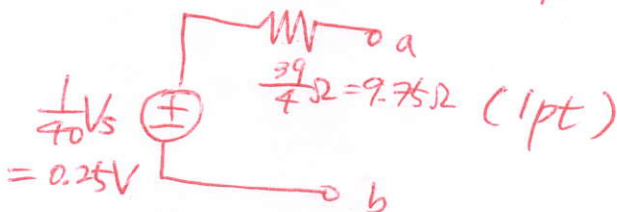

SOLUTIONS

For parts (b) to (d), please use the values $V_{TH} = 5\text{ V}$ and $R_{TH} = 1\text{ k}\Omega$ INSTEAD of the values you found in part (a).

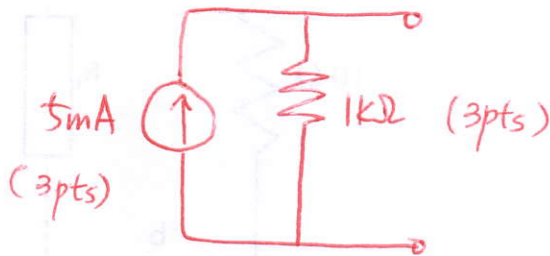b.) Find the Norton equivalent between a and b [6 pts]



c.) Based on your answer in part (b), find the optimal R_L such that the power delivered to R_L is maximized. [3 pts]

$$R_L = R_{TH} = 1\text{ k}\Omega \quad (3\text{pts})$$


d.) Based on your answer to part (c), what power is dissipated by R_L ? [3 pts]

$$P = I^2 R = \left(\frac{5}{2\text{k}}\right)^2 \cdot 1\text{k} = 6.25\text{ mW} \quad (3\text{pts})$$

SOLUTIONS

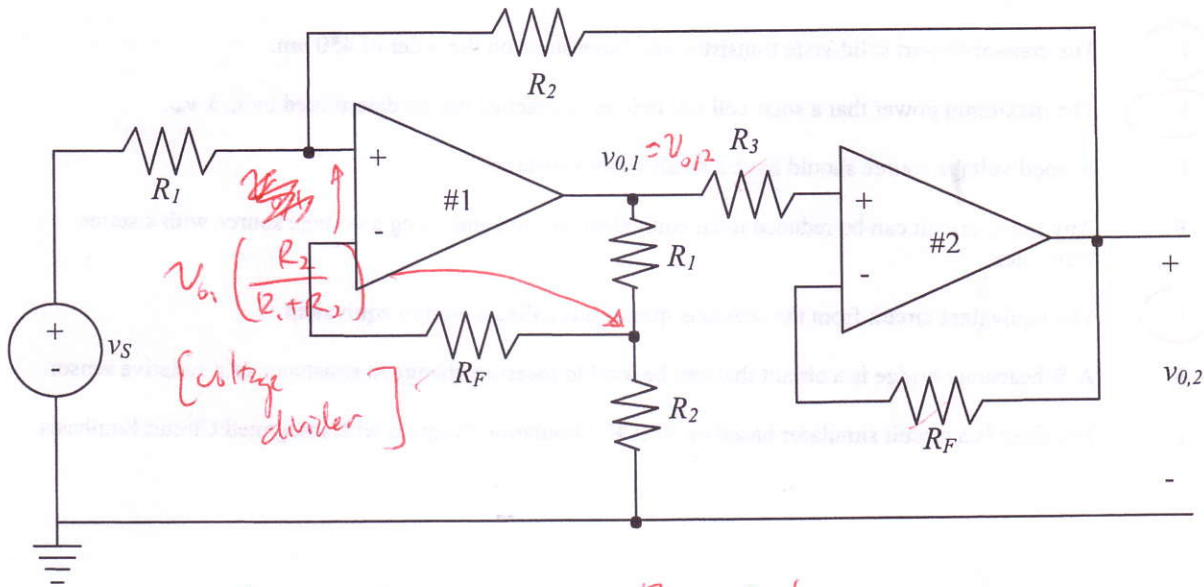Problem 4 [20 points]: Op Amp Circuit

Consider the circuit below. Assume that both op-amps are ideal.



No voltage drop across R_3, R_F !

- a) Write the KCL expression at the non-inverting input of op-amp #1. Be sure to label any new variables you create on the circuit diagram above. [8 pts]

$$\frac{v_s - v_{o1} \left(\frac{R_2}{R_1 + R_2} \right)}{R_1} + \frac{v_{o2} - v_{o1} \left(\frac{R_2}{R_1 + R_2} \right)}{R_2} = 0$$

$$\Rightarrow R_2 [v_s - v_{o1} (A)] + R_1 [v_{o2} - v_{o1} (A)] = 0$$

- b) Find the expression for the overall gain, $G = v_{o2}/v_s$ in terms of the listed parameters. [12 pts]

$$v_{o1} = v_{o2}$$

$$\Rightarrow R_2 [v_s - v_{o2} (A)] + R_1 [v_{o2} - v_{o2} (A)] = 0$$

$$v_{o2} [A(R_2 + R_1) - R_1] = R_2 v_s$$

$$\Rightarrow \frac{v_{o2}}{v_s} = \frac{R_2}{R_2 + R_1} = 1 - \frac{R_2}{R_1}$$

-2 pts for extra terms in KCL

+4 pts for each correct term KCL

+4 pts for voltage divider or KCL @ right node
+4 for $v_{o2} = v_{o1}$

+4 for correct expression

SOLUTIONS

Problem 5 [16 points]: EE Technology and Circuit Basics

True or False Questions. Select only ONE answer. [2 pts each]

- ☒ T ☐ F Moore's Law describes the phenomenon where the number of transistors on a computer chip doubles every 1.5 to 2 years.
- ☐ T ☒ F The state-of-the-art solid-state transistor has dimensions on the order of $450\text{ }\mu\text{m}$.
- ☐ T ☒ F The maximum power that a solar cell can deliver in practice can be determined by $i_{sc} \times v_{oc}$.
- ☒ T ☐ F A good voltage source should have a small series resistance.
- ☒ T ☐ F Any linear circuit can be reduced to an equivalent circuit comprising a voltage source with a series resistance.
- ☐ T ☒ F The equivalent circuit from the previous question is called a Norton equivalent.
- ☒ T ☐ F A Wheatstone bridge is a circuit that can be used to measure change in resistance of a resistive sensor.
- ☒ T ☐ F Multisim is a circuit simulator based on SPICE: Simulation Program with Integrated Circuit Emphasis.