

EE40 Spring 2011 Midterm 1 Solutions


Problem 1:

Identical to a problem from last year's midterm and a problem from HW6. The most common mistake was to assume that the voltmeter was a short, which is not true. Voltmeters have high resistance; ammeters have low resistance!

5. Suppose you stand barefoot on a wet floor with a hand-held digital voltmeter (DVM) in one hand. You insert one probe of the DVM into the hot output of a 110 V outlet and touch the other probe with your free hand.

Hypothetical experiment—don't try this!

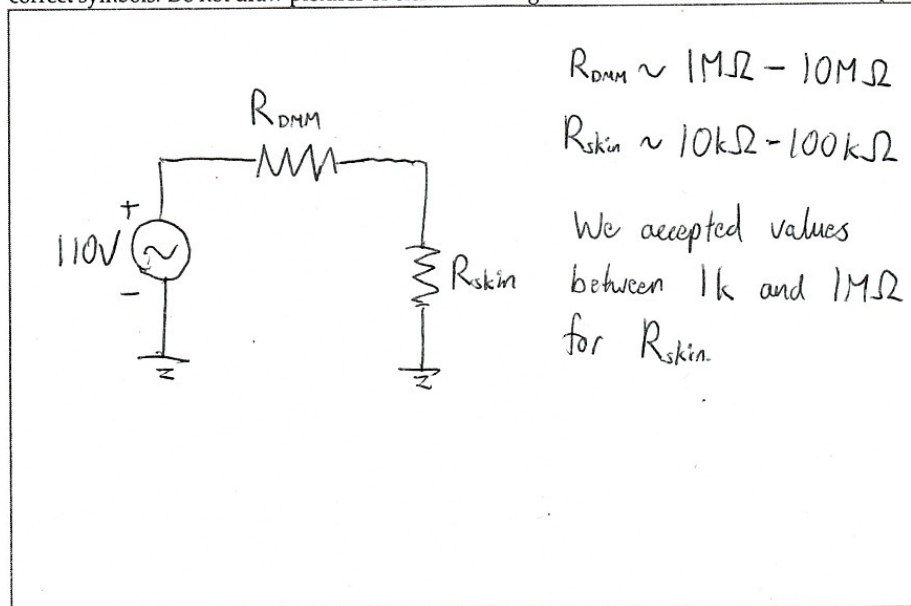- a) Draw a circuit schematic of the situation. Use only circuit elements—sources and resistors—and their correct symbols. Do not draw pictures of elements. Assign reasonable values to all circuit components.



10 pts.
3

- b) Would you get hurt? Explain!

No. R_{DMM} and R_{skin} form a voltage divider. So, voltage across skin is relatively small.

$$V_{skin} \sim \frac{R_{skin}}{R_{skin} + R_{DMM}} \sim \frac{10k}{10k + 1M} \approx 1.1V, \text{ which is safe.}$$


Or, since R_{DMM} and R_{skin} are in series,

$$I < \frac{V}{R_{DMM}} = \frac{110V}{1M\Omega} \approx 0.11mA, \text{ which won't hurt you.}$$

10 pts.
4

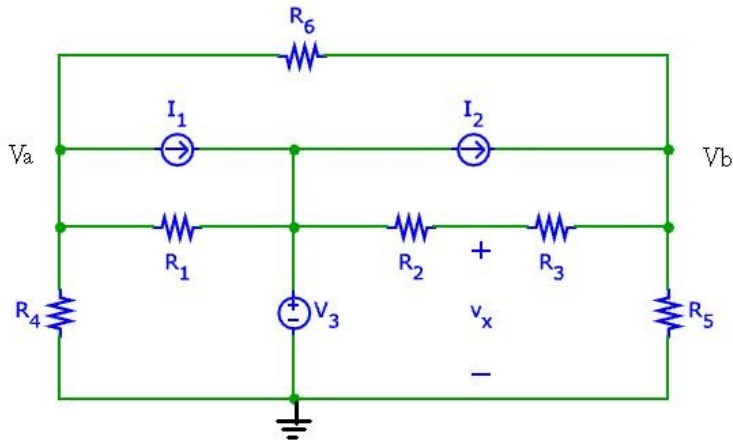Problem 2:

Identical to a problem from HW6. The easiest way to do this problem is Node Voltage Analysis.



$$\frac{V_a - V_b}{R_6} + I_1 + \frac{V_a - V_3}{R_1} + \frac{V_a}{R_4} = 0$$

$$\frac{V_a - V_b}{R_6} + I_2 + \frac{V_3 - V_b}{R_2 + R_3} = \frac{V_b}{R_5}$$

2 equations, 2 unknowns. Most of you did this part right. Some of you also wrote an equation for V_x , giving you 3 equations and 3 unknowns, which is ok too.

One mistake we saw pretty frequently was writing a KCL at V_3 . This doesn't work because you can't easily express the current running through V_3 .

Some of you tried other techniques such as mesh current analysis (5 equations, 5 unknowns) and superposition. In general, success rates using these techniques were pretty low.

Solving these equations algebraically gets pretty messy so most of you decided to proceed numerically. The values for V_a and V_b are:

Version	V_a	V_b
1	1.92V	11.38V
2	-2.19V	13.92V
3	0.75V	10.35V

From there, we can write:

$$V_x = V_3 + \frac{(V_b - V_3) R_2}{R_2 + R_3}$$

Quite a few of you just did a voltage divider without offsetting the result by V_3 . The correct numerical answers are:

Version	V _x
1	3.84V
2	6.78V
3	8.67V

Problem 3:

Surprise, surprise! Another problem straight from homework... the solution is reproduced below:


We note that the circuit can be greatly simplified through source transformations. Start off by transforming I_1 into a voltage source.

$$V_1 = I_1 R_1$$

V_1 and V_2 as well as R_1 and R_2 can now be added in series.

$$V_{12} = I_1 R_1 + V_2$$

$$R_{12} = R_1 + R_2$$

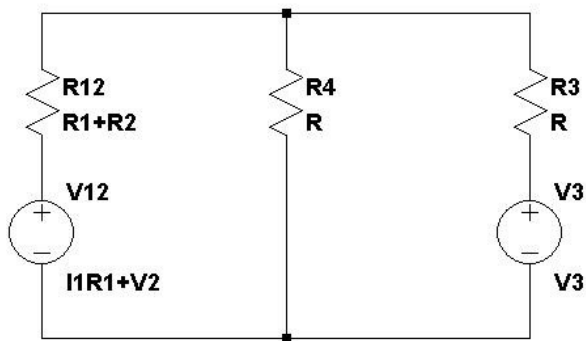


Next, we note that if we transform the two voltage sources into current sources, we can combine them in parallel.

$$I_{12} = \frac{V_{12}}{R_{12}} = \frac{I_1 R_1 + V_2}{R_1 + R_2}$$

$$I_3 = \frac{V_3}{R_3}$$

$$I_{tot} = I_{12} + I_3 = \frac{I_1 R_1 + V_2}{R_1 + R_2} + \frac{V_3}{R_3}$$
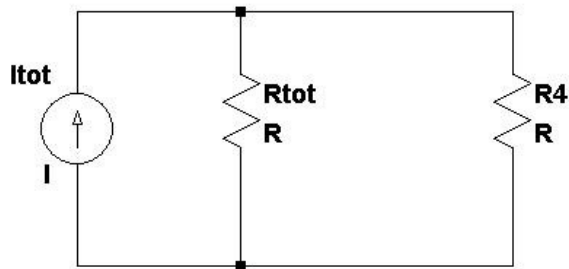
$$R_{tot} = R_{12} \parallel R_3 = \frac{(R_1 + R_2) R_3}{R_1 + R_2 + R_3}$$



Some of you might be tempted to combine $R4$ into R_{tot} , to simplify the circuit even further. However, we want to leave $R4$ intact because our final objective is to find the current flowing through $R4$. We lose that information if we lump $R4$ into everything else!

Finally, we note that all we're left with is a current divider. Thus,


$$i_x = I_{tot} \cdot \frac{R_{tot}}{R_{tot} + R_4}$$

The numerical answers for I_{tot} , R_{tot} , and i_x are:

Version	I_{tot}	R_{tot}	i_x
1	5.25mA	3.2kOhm	1.50mA
2	3.57mA	3.94kOhm	1.57mA
3	10.4mA	0.875kOhm	1.16mA

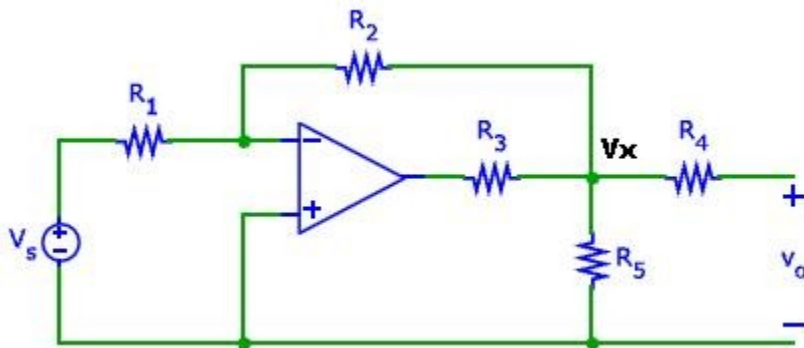Problem 4:

The circuit in this problem is similar to one you analyzed for one of the practice assignments.




In particular, we note that since the op-amp can output any amount of current, the voltage V_x is simply:

$$V_x = V_s \cdot \frac{R_2}{R_1}$$

If you don't believe this, write the KCL equation at the negative terminal of the op-amp.

In addition, R_5 has no effect on the voltage at V_x .

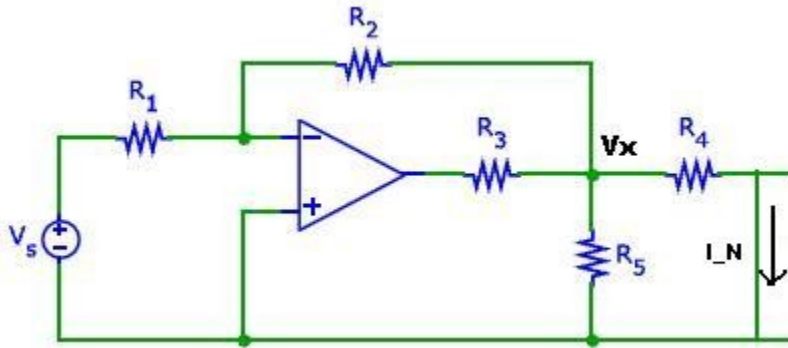With these observations, this problem becomes trivial. We want to model the circuit as a current source in parallel with a resistor. To find I_N , we short the output and find the current.



$$I_N = \frac{V_x}{R_4} = V_s \cdot \frac{R_2}{R_1 R_4}$$

To find R_N , we find the open circuit voltage.

$$V_{OC} = V_x = V_s \cdot \frac{R_2}{R_1}$$


$$R_N = \frac{V_{OC}}{I_N} = R_4$$

An alternative method of finding R_N is to turn off V_s and note that the resistance seen at the output is simply R_4 .

Version	I_N	R_N
1	0.544mA	9.8kOhm
2	3.36mA	1.1kOhm
3	3.42mA	9.5kOhm

Problem 5:

This is the approach we were expecting:

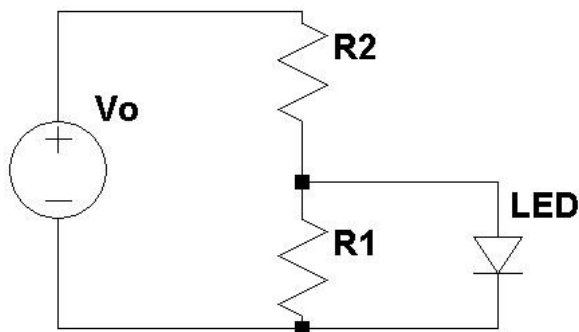

We need at least 2V to get any current through the LED. Thus, there is no way the LED can be on at $V_o=1V$ so we don't have to worry about that condition. As for the other condition, we match the range of "bright on" to the V_o range. In other words,

$$I_D = 1.5mA \text{ when } V_o = 3V$$

$$I_D = 4.5mA \text{ when } V_o = 5V$$

From the graph, we see that 2.5V gives 1.5mA of current and 3.5V gives 4.5mA of current. From this, we can write two equations (is this starting to look like a homework problem?)

Case 1 ($V_o=3V$):

$$\frac{3V - 2.5V}{R_2} = \frac{2.5V}{R_1} + 1.5mA$$

Case 2 ($V_o=5V$):

$$\frac{5V - 3.5V}{R_2} = \frac{3.5V}{R_1} + 4.5mA$$


Isolating for R_2 for both equations the equating the two:

$$\frac{0.5V}{\left(\frac{2.5V}{R_1} + 1.5mA\right)} = \frac{1.5V}{\left(\frac{3.5V}{R_1} + 4.5mA\right)}$$

$$\frac{1.75}{R_1} + 0.00225 = \frac{3.75}{R_1} + 0.00225$$

$$\frac{1.75}{R_1} = \frac{3.75}{R_1} \text{ (what?!)}$$

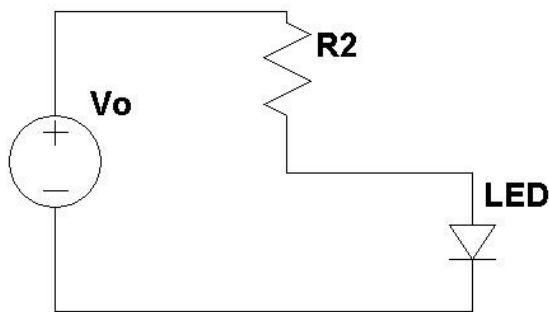Some of you might have gotten to this point and given up on this approach. Think! How could the above expression possibly hold? ... What if R_1 is infinity? Remember that an infinite resistance is just an open circuit. Thus, we can just remove R_1 entirely.




Plugging back into one of the original equations:

$$R_2 = \frac{0.5V}{\left(\frac{2.5V}{R_1} + 1.5mA\right)} = 333\Omega$$

Yeah, the solution is just a 333-Ohm series resistor.

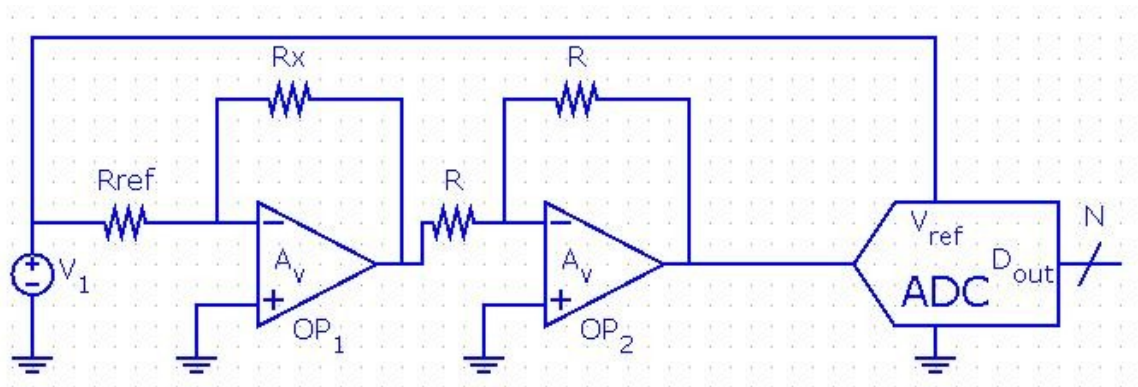Problem 6:

We might have done you a great disservice by drawing R_X outside the box. This is the solution we were expecting:



The output of the first stage is:

$$-V_1 \cdot \frac{R_X}{R_{ref}}, \text{ which we note increases linearly with } R_X$$

The second stage inverts the signal, since we want the input to be positive. Thus, the input to the ADC is:

$$V_{in} = V_1 \cdot \frac{R_X}{R_{ref}}$$

$$D_0 = 1000 \cdot \frac{V_{in}}{V_{ref}} = 1000 \cdot \frac{R_X}{R_{ref}}, \text{ which is what we want}$$

We saw some pretty creative solutions. A good fraction of you reversed the positions of R_X and R_{ref} but connected V_1 to V_{in} and the output of the opamp to V_{ref} . This works great on paper and we gave full credit for this solution. In practice, however, we generally want V_{ref} to be constant.

Some of you tried to use V_1 as a dual supply. Unfortunately, this approach doesn't work because it results in a floating source.

Moral of this midterm: Do the homework!