



University of California
College of Engineering
Department of Electrical Engineering
and Computer Sciences

J. Rabaey

WeFr 2-3:30pm

Fr, February 19, 6:30-8:00pm

EECS 141: SPRING 10—MIDTERM 1

NAME	Last	First
-------------	------	-------

SID	Solution
------------	-----------------

Last Updated on 2010/02/24

Problem 1 (15):

Problem 2 (12):

Problem 3 (15):

Total (42)	
-------------------	--

[PROBLEM 1] CMOS NON-INVERTING BUFFER (15 pts)

The following circuit can be seemed as a “DIGITAL NON-INVERTING BUFFER”.

 


Fig.1 (a) DIGITAL BUFFER & VTC

(a) (3pts) Compute V_{IL} , V_{IH} , V_{OL} , V_{OH} , NM_L , and NM_H .

$$NM_L = V_{IL} - V_{OL} = 0.1V$$

$$NM_H = V_{OH} - V_{IH} = 0.3V$$

(i) V_{IL}	= 0.4V (0.5pts)
(ii) V_{IH}	= 0.7V (0.5pts)
(iii) V_{OL}	= 0.3V (0.5pts)
(iv) V_{OH}	= 1.0V (0.5pts)
(v) NM_L	= 0.1V (0.5pts)
(vi) NM_H	= 0.3V (0.5pts)

 


Fig.1 (b) One-stage DIGITAL BUFFER with 100fF C_L

(b) (6pts) For Fig.1.(b), the output voltage, V_{OUT} , is initially discharged, $V_{OUT}=0$. You may ignore the intrinsic capacitance, or diffusion capacitance, of the buffer.

Find the energy dissipated in the buffer during the first 0 to 1.2V step input (i), **First E_{DISS}** .

Then, after the output reaches its final value, a 1.2V to 0 step is applied to the input (ii). Find the energy dissipated in the buffer, **Second E_{DISS}** .

A second 0 to 1.2V step follows (iii). Find again the energy dissipated in the buffer (**Third E_{DISS}**).

- i) $1^{st} E_{DISS} = E_{SUPPLY} - E_{STORED}$, $V_{OUT}: 0V \rightarrow 1.0V$ (0.8pts)
 $= C_L * V_{DD} * (1.0) - \frac{1}{2} * C_L * (1.0)^2$ (1pts) $= 100f * (1.2 - 0.5) = 70fJ$ (0.2pts)
- ii) $2^{nd} E_{DISS} = E_{STORED} - E_{REMAINED}$, $V_{OUT}: 1.0V \rightarrow 0.3V$ (0.8pts)
 $= \frac{1}{2} * C_L * (1.0)^2 - \frac{1}{2} * C_L * (0.3)^2$ (1pts) $= 50f * (1 - 0.09) = 45.5fJ$ (0.2pts)
- iii) $3^{rd} E_{DISS} = E_{SUPPLY} - E_{STORED}$, $V_{OUT}: 0.3V \rightarrow 1.0V$ (0.8pts)
 $= C_L * V_{DD} * (1.0 - 0.3) - \frac{1}{2} * C_L * [(1.0)^2 - (0.3)^2]$ (1pts)
 $= 100f * 1.2 * 0.7 - 50f * (1 - 0.09) = 38.5fJ$ (0.2pts)

(i) $1^{st} E_{DISS} = 70fJ$ (0.2pts)

(ii) $2^{nd} E_{DISS} = 45.5fJ$ (0.2pts)

(iii) $3^{rd} E_{DISS} = 38.5fJ$ (0.2pts)


 


Fig.1 (c)

- (c) (4 pts) One engineer tried to develop a transistor-level implementation of the buffer as shown in Fig.1(c). Draw the VTC of the circuit where V_{IN} goes from 0V to 1.2V and then goes back to 0V. Here, the $V_{TN}=|V_{TP}|=0.2V$, $R_{OFF}=\infty$, and no body effect, that is the threshold voltage is not dependent upon the voltage of the body.

 

Assume that the input is at 0 and the output is at $|V_{TP}|$. As the input is increased, the output will stay constant until the NMOS device turns on. That will occur at $V_{IN}=|V_{TP}|+V_{TN}$. The upper transistor behaves as a source follower and will pull the output along as the input rises until the output reaches $V_{DD}-V_{TN}$. However, as the input is reduced in value the output stays at its high value until the PMOS device turns on. This occurs at $V_{IN}=V_{DD}-(|V_{TP}|+V_{TN})$. Then the PMOS device acts as a source follower and the output drops linearly to $|V_{TP}|$ as the input is reduced.

VIL=0.4 (1pts), VIH=0.8 (1pts), VOL=0.2 (1pts), VOH=1.0 (1pts)

(d) (2pts) Can the gate of Fig 1.c still be considered a digital gate (or, is it still regenerative)? Explain in a couple of words why or why not.

A digital gate. (1pts)

The gain of the circuit is close to unity, but the circuit still has noise margin. Therefore, it has noise rejection properties. (1pts)

[PROBLEM 2] RING OSCILLATOR (12pts)

Consider the 5-stage ring oscillator shown in Fig.2a, which is used to generate a clock signal. The input gate capacitance of a minimum-sized inverter (size=1) is $C_{IN}=10fF$, while $R_{ON,N}=R_{ON,P}=7.22k\Omega$, and $R_{OFF}=\infty$. Assume that the input capacitance is proportional to its size, and R_{ON} is inversely proportional to its size. The diffusion capacitance, or intrinsic capacitance, of inverter is the same as the gate capacitance, $\gamma=1$. Ignore resistance and capacitance of the wires between the inverters.



 


Fig.2 (a) 5-stage Ring Oscillator

 - (a) (6pts) Determine the oscillation frequency of this circuit at V_{OUT} for $R=1$ (that is, using unit inverters). Determine also the power dissipation of the circuit P_{SUPPLY} for $V_{DD} = 1.2V$. You should take into account the gate and diffusion capacitances.


 
$$t_{inv} = \ln(2) \cdot R_{ON,MIN} \cdot C_{IN,MIN} = \ln(2) \cdot 7.22k \cdot 10f = 50.05pS \cong 50pS \text{ (2pts)}$$



Signal should turn twice of 5-stage inverter chain to make one cycle.

$$T = 2 \cdot 5 \cdot t_{P,INV} \text{ (2pts)} = 10 \cdot t_{inv} \cdot (\gamma + f) = 10 \cdot 50p \cdot (1+1) = 1nS \text{ (0.3pts)}$$

$$F = 1/T = 1GHz$$

$$P_{SUPPLY} = C_{TOT} \cdot V_{DD}^2 \cdot f = 100f \cdot 1.2^2 \cdot 1G = 144\mu W \text{ (0.3pts)}$$

,where $C_{TOT} = 5 \cdot (2 \cdot C_R) = 10 \cdot 10f \cdot R = 100f \cdot R = 100fF$ due to $R=1$. (1.4pts)

$$f = 1GHz \text{ (0.3pts)}$$

$$P_{SUPPLY} = 144\mu W \text{ (0.3pts)}$$

- (b) (6pt) Determine the oscillation frequency of ring oscillator and as well as the power dissipation, when the inverters are sized at $R=2$, $R=4$, and $R=8$, respectively. Please normalize your results with respect to $f_{R=1}$ and $P_{SUPPLY,R=1}$.

According to delay equation, the delay is independent of the size of inverter. So, there is no change in cycle even if the size of inverter is changed. **(2pts)**

$$T = 2 \cdot 5 \cdot t_{P,INV} = 10 \cdot t_{inv} \cdot (\gamma + f) \quad \textbf{(0.7pts)}$$

In terms of energy, the energy is linearly proportional to the size of inverter (R). So, the energy is increased by the size of inverter (R). **(2pts)**

$$P_{SUPPLY} = C_{TOT} \cdot VDD^2 \cdot f = 5 \cdot (2 \cdot C_R) \cdot VDD^2 \cdot f \quad \textbf{(0.7pts)}$$

R	$f_R / f_{R=1}$	$P_{SUPPLY,R} / P_{SUPPLY,R=1}$
2	1 (0.1pts)	2 (0.1pts)
4	1 (0.1pts)	4 (0.1pts)
8	1 (0.1pts)	8 (0.1pts)

[PROBLEM 3] COMPLEX LOGIC AND LOGICAL EFFORT (15 pts)

(a) (2pts) Implement the logic function $F = \overline{A \cdot B + C}$ by using a complex static CMOS Gate. Place the PMOS and NMOS driven by input A closest to the output node, F, in your transistor stacks.


 


Fig.3 (a) Complex Gate

 

(b) (3pts) The unit inverter is shown in Fig. 3(b). Assume that $C_D = C_G = 2\text{fF}/\mu\text{m}$. Size the *transistors of the complex gate in (a)* such that the worst cast driving strength for all inputs is the same as a unit inverter. Give the width of all transistors in units of μm . Determine the logical effort for each input?


 


Fig.3 (b) Unit Inverter

 

**Sizes of all transistors:
(In units of μm)**

$W_{pA} = W_{pB} = W_{pC} = 4\mu\text{m}$ (0.5 pts)

$W_{nA} = W_{nB} = 2\mu\text{m}$ (0.5 pts)

$W_{nC} = 1\mu\text{m}$ (0.5 pts)

$LE_A = 2$ (0.5 pts)

$LE_B = 2$ (0.5 pts)

$LE_C = 5/3$ (0.5 pts)

(c) (5 pts) In Fig. 3(c), we insert two unit-sized inverters to drive input A of the complex gate. For the complex gate, use the sizes of transistors that you derived in (b). Assume that $C_D = C_G = 2fF/\mu m$. The delay, $Td1$, measured from **In** to **X** is 40ps. What is the delay, $Td2$, measured from **In** to **Y**?

(Note: If you don't know the answer for (a) and (b), replace the complex gate with a 3-input NOR gate, $F = A + B + C$. Size the transistors of 3-input NOR gate such that the worst cast driving strength for all inputs is the same as a unit inverter.)

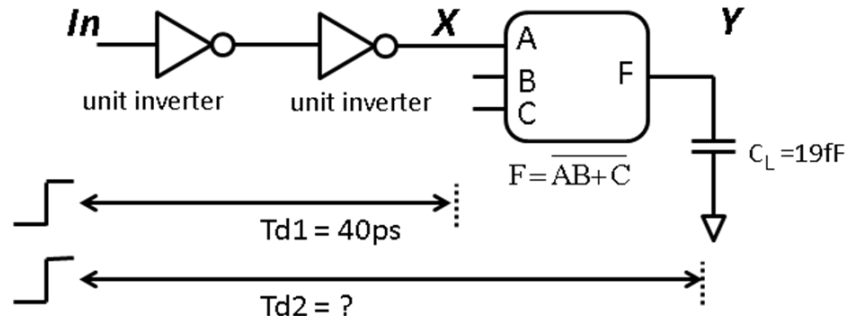


Fig.3 (c) Delay of the Complex Gate

Solution:

$$Td1 = t_{inv} \left[\left(1 + \frac{C_{g_{inv2}}}{C_{g_{inv1}}}\right) + \left(1 + \frac{C_{g_{Complex,inputA}}}{C_{g_{inv2}}}\right) \right] = t_{inv} \left[\left(1 + \frac{6fF}{6fF}\right) + \left(1 + \frac{12fF}{6fF}\right) \right] = 5t_{inv} \quad (2 \text{ pts})$$

$$Td2 = t_{inv} \left[\left(1 + \frac{C_{g_{inv2}}}{C_{g_{inv1}}}\right) + \left(1 + \frac{C_{g_{Complex,inputA}}}{C_{g_{inv2}}}\right) + \left(p + LE \frac{C_L}{C_{g_{Complex,inputA}}}\right) \right] \quad (2 \text{ pts})$$

$$= t_{inv} \left[\left(1 + \frac{6fF}{6fF}\right) + \left(1 + \frac{12fF}{6fF}\right) + \left(\frac{22fF}{6fF} + 2 \cdot \frac{19fF}{12fF}\right) \right] = 11.83t_{inv}$$

$$\frac{Td2}{Td1} = \frac{Td2}{40ps} = \frac{11.83t_{inv}}{5t_{inv}} \rightarrow t_{inv} = 8ps$$

$$\Rightarrow Td2 = 94.67ps \quad (1 \text{ pt})$$

Td2= 94.67ps

(d) (5pts) The complex gate that you designed in (a) is used in the critical path of the logical network shown in Fig. 3(d). Assume that $C_D = C_G = 2fF/\mu m$. What is the total path effort from In to Out? In order to minimize the delay, what should the effective fan-out per stage for this chain of gates be?

(Note: If you don't know the answer in (a) and (b), replace the complex gate with a 3-input NOR gate, $F = A + B + C$.)

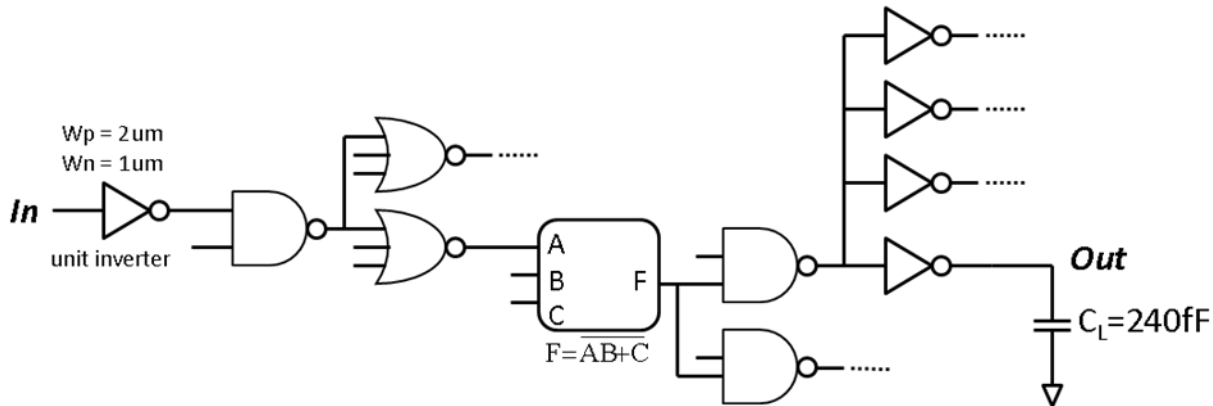


Fig.3 (d) Critical Path of Combinational Logic

Solution:

$$\prod LE = 1 \times \left(\frac{4}{3}\right) \times \left(\frac{7}{3}\right) \times 2 \times \left(\frac{4}{3}\right) \times 1 = \frac{224}{27} = 8.296 \quad (1 \text{ pt})$$

$$\prod B = 1 \times 1 \times 2 \times 1 \times 2 \times 4 = 16 \quad (1 \text{ pt})$$

$$F = \frac{C_L}{C_{in}} = \frac{240 fF}{\left(\frac{2 fF}{\mu m}\right)(2 \mu m + 1 \mu m)} = 40 \quad (1 \text{ pt})$$

$$\text{Path Effort: } PE = (\prod LE)(\prod B)F = \frac{224}{27} \times 8 \times 40 = \frac{143360}{27} = 5039.63 \quad (1 \text{ pt})$$

$$\text{Effective Fan-out: } EF = \sqrt[6]{PE} = \sqrt[6]{5039.63} = 4.18 \quad (1 \text{ pt})$$

$$PE = 5039.63$$

$$EF = 4.18$$